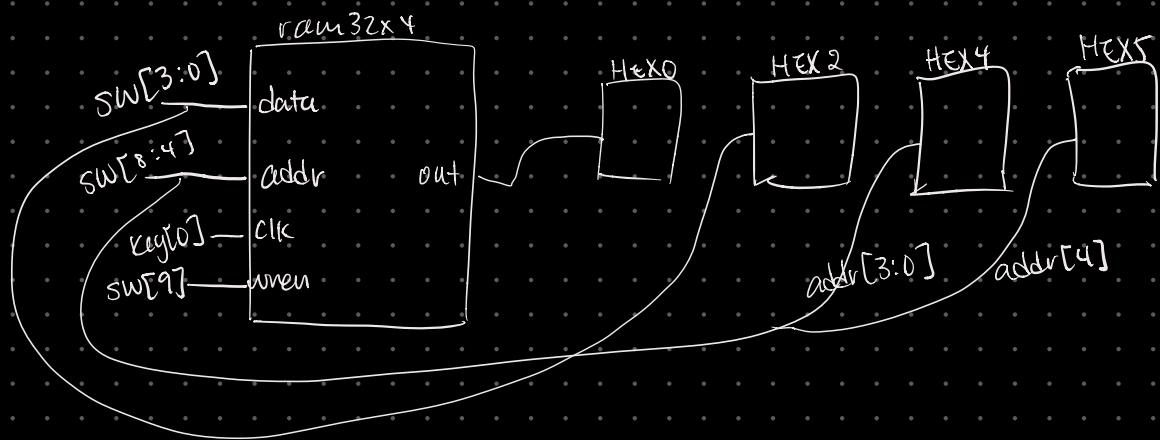


11) Schematic of circuit




P4.2

Display simple images on VGA display

→ Design circuit to draw a filled square on the screen @ any location in any colour

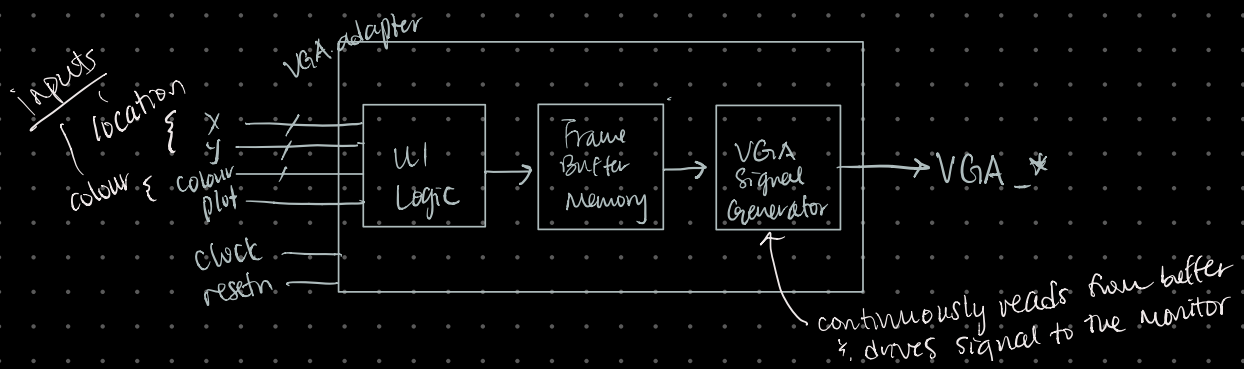VGA adapter module → accepts a set of (x,y) coords (pixel) and a colour



RGB  $\rightarrow$  (1, 0, 1) = Red

(0, 1, 1) = additive G, B colour

KEY[0]: active low reset

SW[9:7]: specify the colour


SW[6:0]: use to input (X, Y)

load: set SW[6:0] to val  
then press KEY[3] to hold  
register w/ X val

X = 8 bits  $\rightarrow$  register 8-bit to hold X val

Y = 7 bits  $\rightarrow$  access only 1st 128 cols

else goes  
to Y

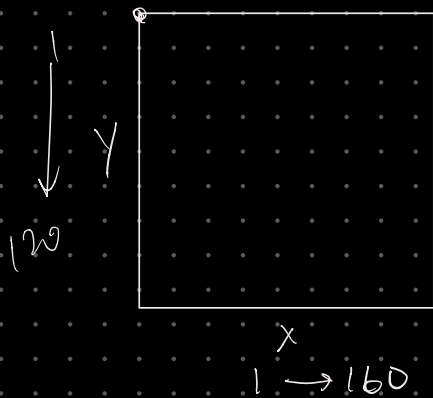


$$2^7 = 128 > 120$$

stores  
X  $\rightarrow$  Y only have 7 bits for inputs (from SW [6:0] signal)

$$\frac{0}{0} \xrightarrow{1} 7 \leq 128$$

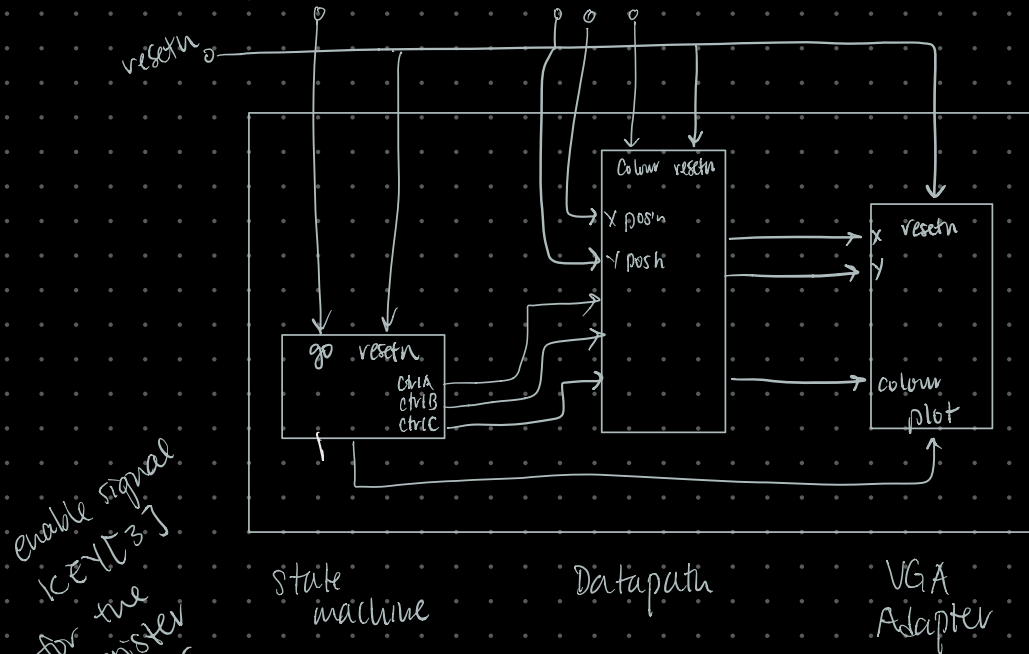Draw filled square when KEY[1] pressed (go)





enable signal  
KEY[3]  
for the  
register  
that holds  
coord X.

\* modify the # of controllers (ctrlA/B/C etc) based on datapath

1) Datapath:

Inputs:  $x, y, \text{column}, \text{ctrl}$  signals


output:  $(x, y)$  to paint

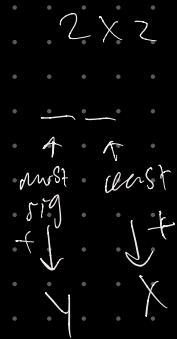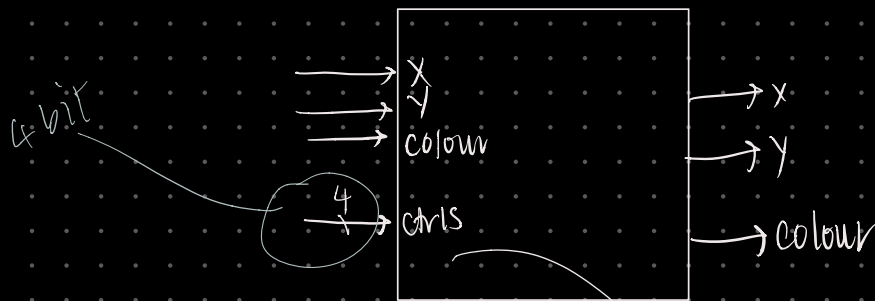

00  
01  
10  
11


$x, y$	$x+1, y$
$x, y+1$	$x+1, y+1$

2) FSM

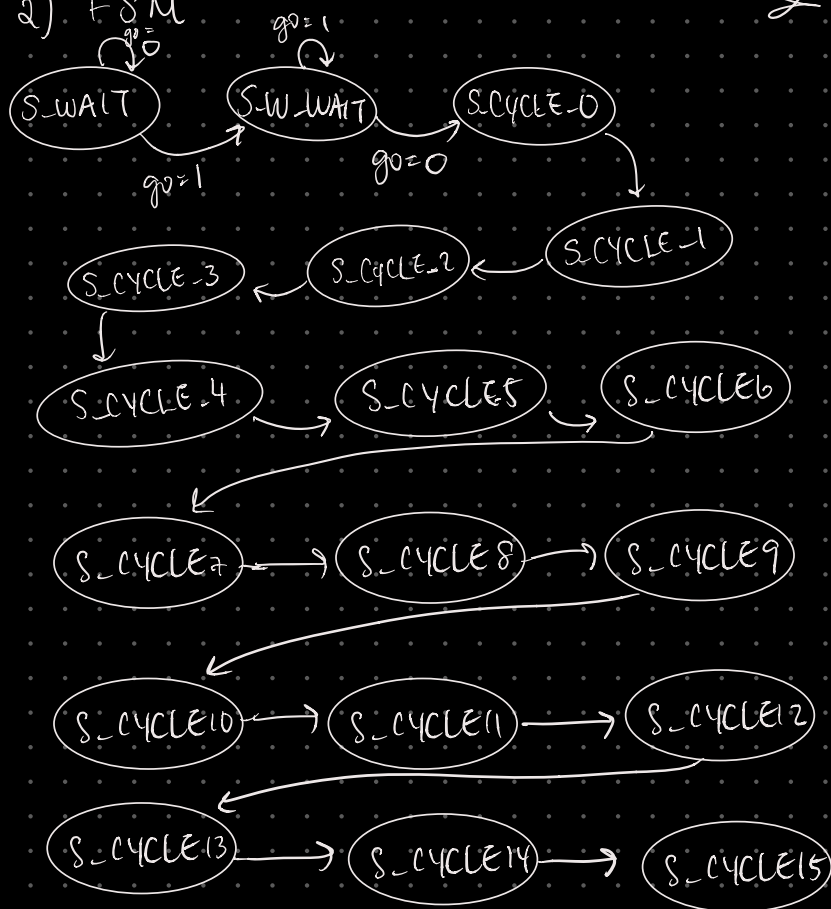

4-bit

$x, y$	$x+1$	$x+2$	$x+3$
$x, y+1$			
$y+2$			
$y+3$			

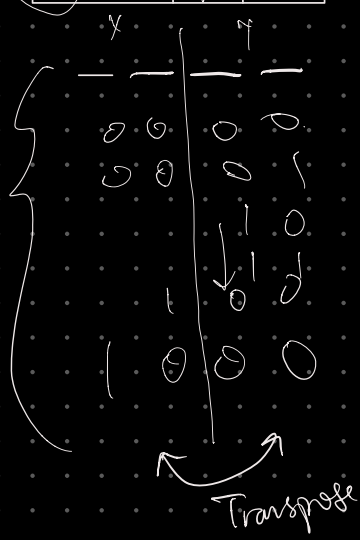

1)

